

# Maharaja Agrasen Institute of Technology, Delhi



## Department of Electrical and Electronics Engineering

### Assignment # 2

Subject Name: Electrical Science




Subject Code: ES-107

Class:

Faculty:

Assignment No	Date Given	Due Date	Mode of Submission	Total Marks	COs mapped
1			Hard copy	10	CO1

Q1. Compute the rms value of the waveform depicted in fig 1(a),1(b),1(c)

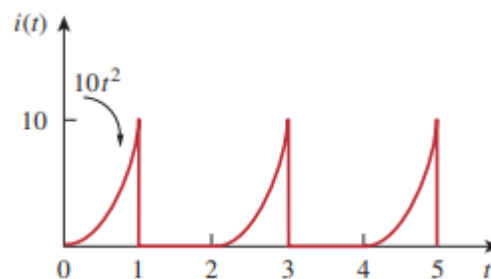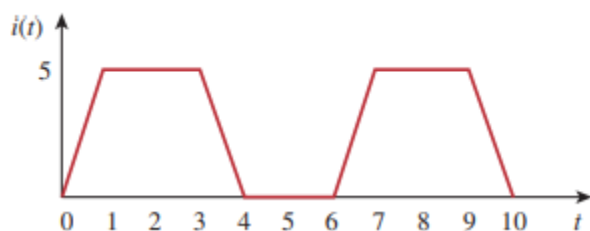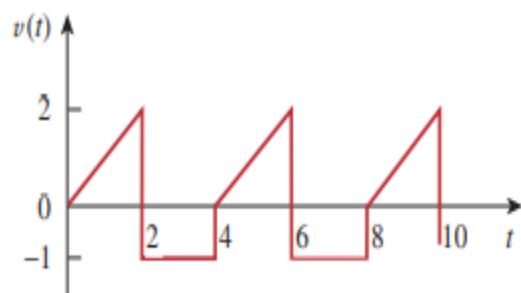

***fig 1(a),1(b),1(c)***

Q2. Find the average value of the waveform shown in Fig. 2(a),2(b),2(c)

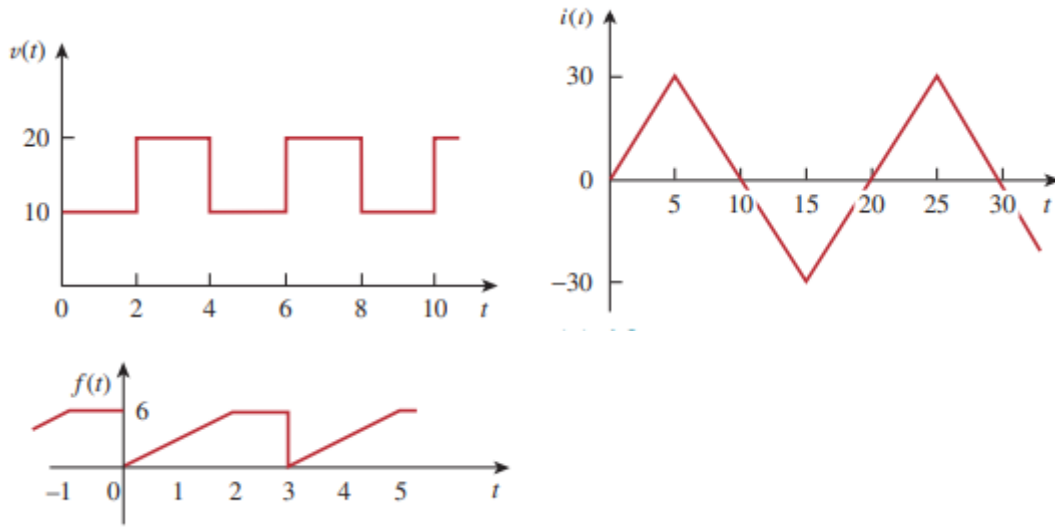


Fig. 2(a),2(b),2(c)

Q3. Find the input impedance of the circuit in Fig.3(a) and 3(b) . Assume that the circuit operates at  $\omega=50$  rad/sec

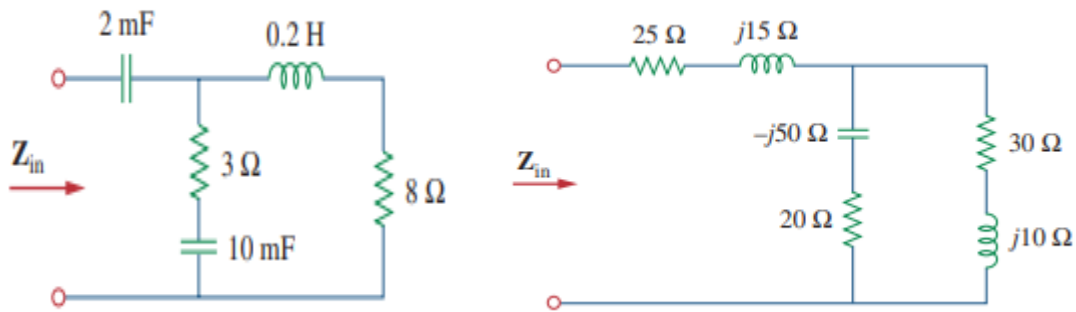


Fig.3(a) and 3(b)

Q4. (a) Determine the power factor of the entire circuit of Fig. 4as seen by the source. Calculate the average power delivered by the source.

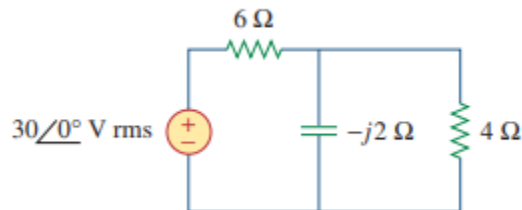


Fig 4

(b) A load  $Z$  draws 12 kVA at a power factor of 0.856 lagging from a 120-V rms sinusoidal source. Calculate: (a) the average and reactive powers delivered to the load, (b) the peak current, and (c) the load impedance

Q5. In the circuit of Fig. 5,  $Z_1 = 60 \angle -30^\circ \Omega$  and  $Z_2 = 40 \angle 45^\circ \Omega$  Calculate the total: (a) apparent power, (b) real power, (c) reactive power, and (d) pf, supplied by the source and seen by the source.

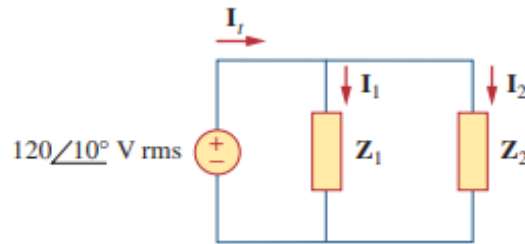


Fig. 5

Q6. Calculate the line currents in the three-wire Y-Y system of Fig 6

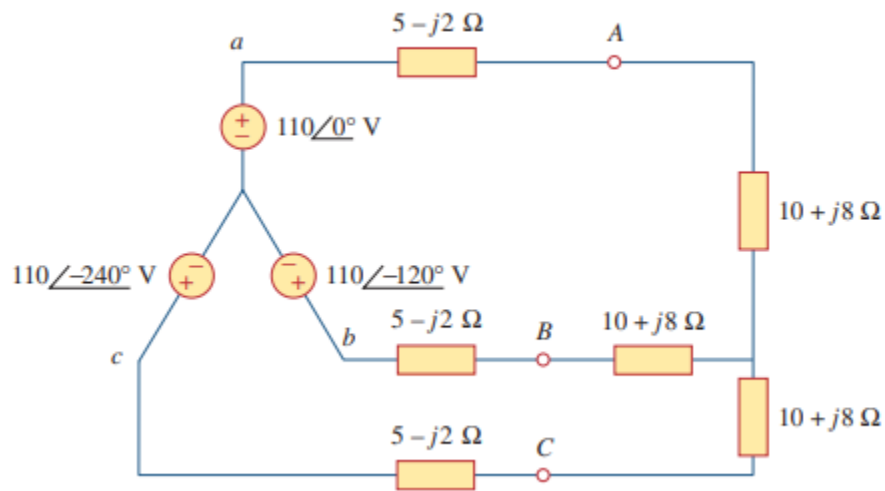


Fig 6

Q7. The three-phase balanced load in Fig. 7 has impedance per phase of  $Z_Y = 8 + j6 \Omega$ . If the load is connected to 208-V lines, predict the readings of the wattmeters and Find  $P_T$  and  $Q_T$

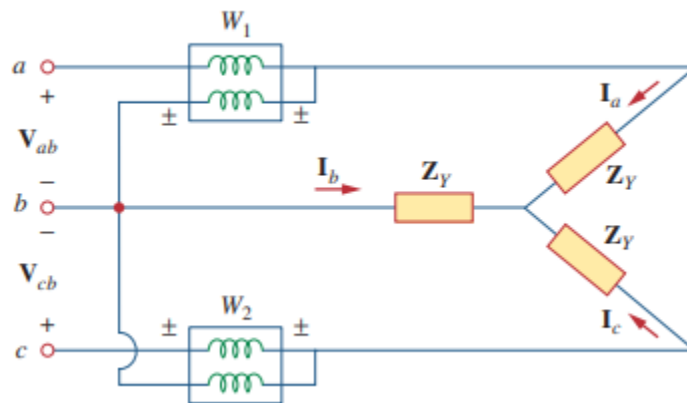


Fig. 7